

# Phase-Locked Loop (PLL) Lab 1

## 1.0 Objective

To build a simple PLL using off-the-shelf CMOS integrated circuit and RC components.

## 2.0 Components, Tools and Instruments

Item	Description	Quantity
1	Project board	1
2	74HC4046 integrated circuit	1
3	Resistors (0.25W 5%): 470 $\Omega$	1
4	Resistors (0.25W 5%): 1000 $\Omega$	1
5	Resistors (0.25W 5%): 3300 $\Omega$	1
6	Resistors (0.25W 5%): 10000 $\Omega$	1
7	Capacitor (ceramic, 50V, 10%): 100pF	1
8	Capacitor (ceramic, 50V, 10%): 1nF	2
9	Capacitor (ceramic, 50V, 10%): 10nF	2
10	Capacitor (ceramic, 50V, 10%): 0.1 $\mu$ F	1
11	Capacitor (Electrolytic, 16V, 0%): 10 $\mu$ F	1
12	Digital sampling oscilloscope (min 50 MHz bandwidth), 2 channels	1
13	Power supply (DC)	2
14	Function generator (1 kHz to 10 MHz)	1
15	Single-core wire (red, blue and black)	1 reel for each color
16	Wire cutter	1
17	Tweezers	1
18	Pen knife	1
19	Long-nose pliers (optional)	1

## 3.0 Introduction

In this simple exercise you would build a phase-locked loop (PLL) using the popular CMOS integrated circuit (IC) 74HC4046. This IC has a built-in relaxation voltage-controlled oscillator (VCO) and three phase detectors (PD): e.g., an XOR gate PD, a RS flip-flop PD and a PFD with charge pump. In this lab we would utilize the XOR gate PD and the PFD to build a PLL. The block diagram of the 74HC4046 is shown in Figure 1.


 



Figure 1 – 74HC4046 block diagram.

#### 4.0 Part 1: XOR Gate PLL

Connect up the circuit as shown in Figure 2 on a project board. Be careful in handling the 74HC4046 IC as it is susceptible to electrostatic discharge damage. Use a tweezers or long-nose plier to pick up the IC. An example of the completed PLL is shown in Figure 3. Keep your circuit tidy, this will make debugging easy. One way to maintain neatness is to use the shortest connecting wire as possible, and to use the upper and lower rows of the project board for  $V_{cc}$  and GND buses (see Figure 3).

 

**Figure 2** – PLL schematic using XOR gate PD.

 

**Figure 3** – The hardware based on schematic of Figure 2.


In this schematic,  $R_2$  and  $C_4$  determine the built-in VCO characteristics. These values allow the VCO oscillation frequency to vary from roughly 450 kHz to 3 MHz, for an input voltage of 0.5 V to 5V. Note that the oscillation range of the built-in VCO is highly dependent on the power supply voltage to the IC, and can vary as much as 100% for supply variation between 4.5V to 6.0V. Capacitor  $C_3$  serves to stabilize the potential on pin 12 of  $U_1$  (This pin is to be left as open circuit). Pin 2 of  $U_1$  is the output of the XOR gate PD while pin 3 is the common input to all the internal PDs of the 74HC4046.

### Step 1 – Measure the VCO gain

Open the PLL loop by disconnecting pin 9 of  $U_1$ . Power up the circuit with a DC power supply, setting the output voltage to 6.0V. Connect pin 9 of  $U_1$  to a second DC power supply. Vary the second power supply output voltage from 0.5 V to 4.5 V in 0.5 V step. Record the frequency observed from the VCO's output. Plot a graph relating the frequency of the VCO's output versus VCO input. Calculate  $k_o$ . A sample result is shown in Table 1.


**Table 1** – Sample measurement of  $f_{vco}$  versus  $V_o$ .

$V_o$ / Volts	$f_{vco}$ / kHz
1.1	470
1.7	700
2.0	870
2.5	1000
3.0	1360
3.4	1600
3.9	2000

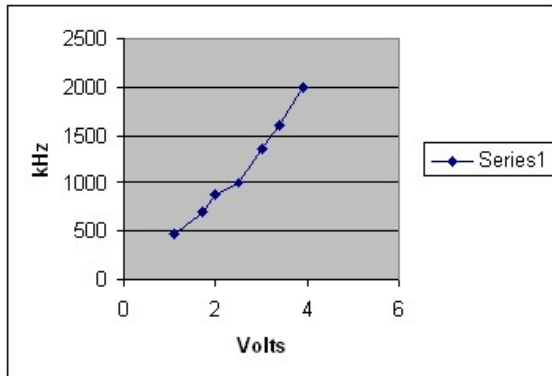


### Step 2 – Connect signal generator – Phase locked

Setup a signal generator to produce a 50% duty cycle square wave with peak-to-peak voltage of around 4.0 V and frequency of 1.5 MHz. Connect the output of the signal generator to pin 14 of  $U_1$  via coupling capacitor  $C_1$ . The PLL should immediately lock to the input signal. Observe the voltage  $V_o$ ,  $V_{in}$  and  $V_{vco}$  during phase-locked. A sample measurement is shown below. Note that  $V_{in}$  leads  $V_{vco}$  in phase. This phase difference, together with the operation of the XOR gate and RC filter results in a voltage  $V_o$  with a ripple at a certain dc average value.

 

**Figure 4** – The input voltage to the VCO,  $V_o$  and the input signal  $V_{in}$  versus time.

 

**Figure 5** – VCO's output  $V_{vco}$  and  $V_{in}$  versus time.


### Step 3 – Tracking mode observation and hold-in range measurement

Now you can increase and decrease the frequency of the input signal and watch the VCO tracks the input signal. Measure the lock or hold-in range ( $f_H$ ) of this PLL and compare this with theory.






Repeat Step 2 and Step 4 of Part 1 for this PLL. After this as an interesting experiment change  $C_2$  to 1 nF, see if the PLL is stable. Figure 7 shows a sample measurement of the VCO's output and  $V_{in}$  signals during phase-locked at 1.5 MHz. Trace 2 is the VCO output and Trace 1 is  $V_{in}$ . Figure 8 shows the spike at the charge pump output due to mismatch within the positive and negative current source and non-ideal properties of the PFD.

 


**Figure 7** – Comparison of  $V_{vco}$  and  $V_{in}$  during phase-locked at 1.5 MHz.

 

**Figure 8** – Voltage spikes at the charge pump output during phase-locked at 1.5 MHz.


### Appendix - Extra Observation for PFD with Charge Pump PLL

It is discovered that the output of the VCO exhibits significant jitter during tracking mode. Although the VCO frequency seems to track the input signal  $V_{in}$ 's frequency, there is some random jitter on the VCO waveforms. Upon closer inspection the author confirms that this is due to non-ideal behavior of the PFD with charge pump of 74HC4046. When the static phase error  $\theta_e$  between the input signal and VCO is very small (as in during phase-locked), the average dc voltage of the PFD with charge pump exhibit nonlinear behavior known as the 'dead-zone' or cross-over distortion. This is largely due to the internal propagation delay of the PFD components. Figure A1 shows an example of cross-over distortion measurement taken from Chapter 5 of the book by *W. F. Egan*, "Frequency synthesis by phase lock", 2000 John-Wiley & Sons. Figure A2 is the capture waveforms of the VCO output and  $V_o$  at  $f_{in} = 1.00$  MHz. Note the jitter and the periodic up and down spike, causing the VCO output to jitter. A display persistence of 1 second is used to show both up and down voltage spike in one screen shot.

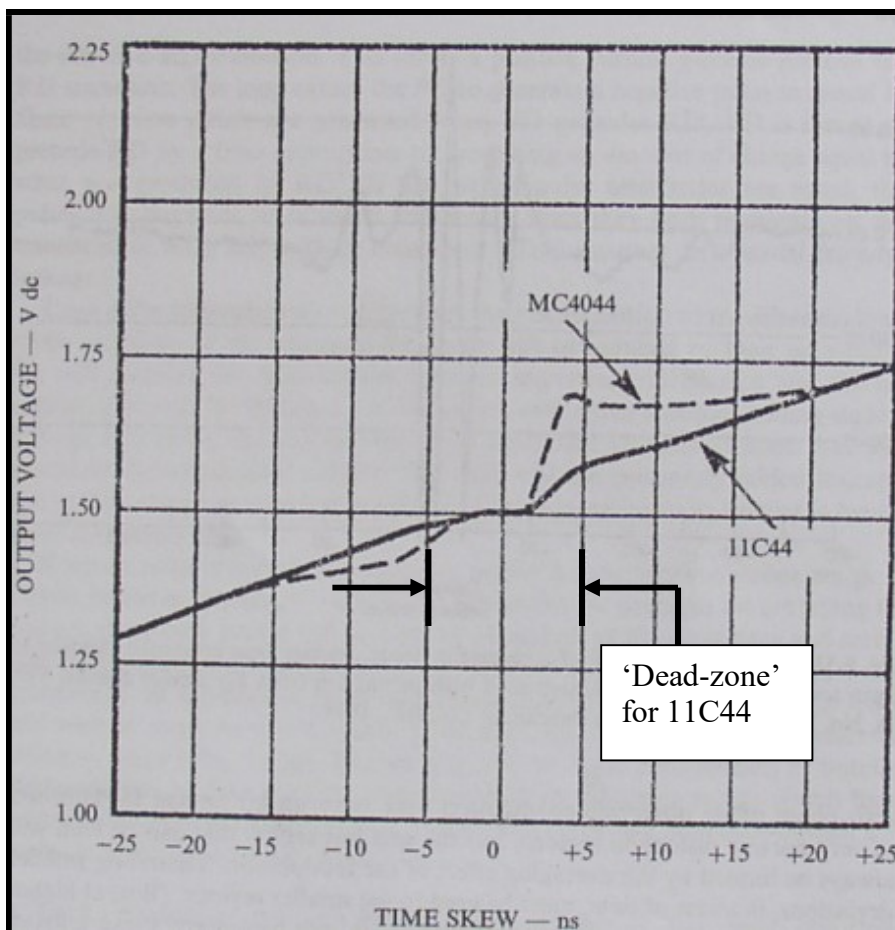


**Figure A1** – Crossover distortion of some PFD with charge-pump, from the datasheet for 11C44, ©Fairchild Semiconductor Corporation, 1975. From *W. F. Egan*, "Frequency synthesis by phase lock", 2000 John-Wiley & Sons.



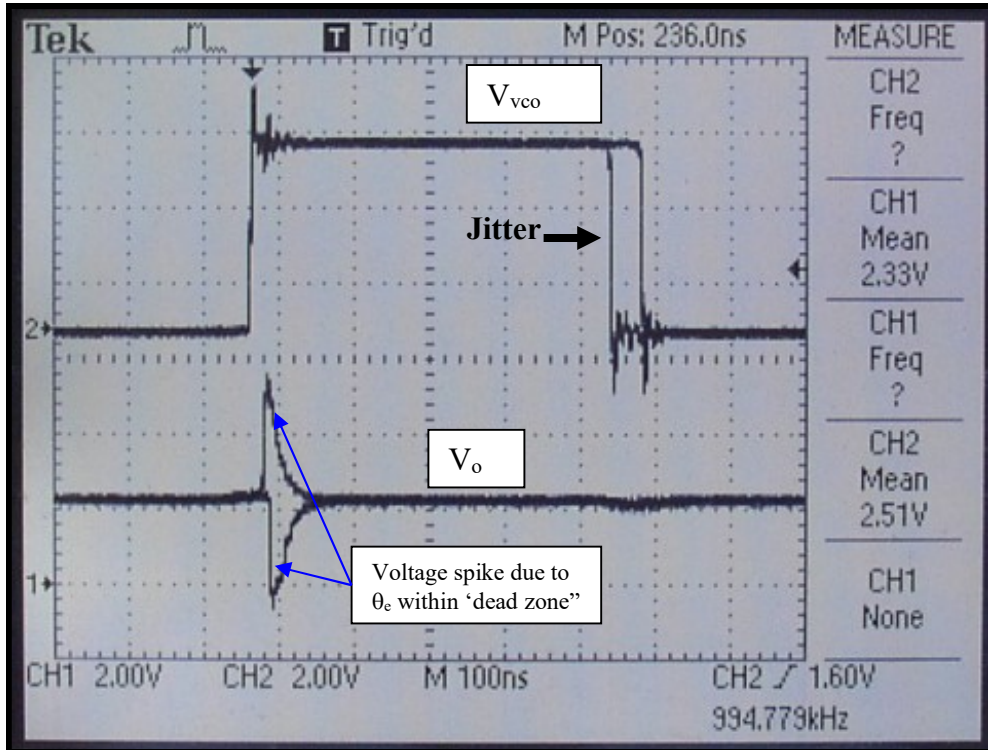


**Figure A2** –  $V_{vco}$  (trigger source) and  $V_o$  waveform, at  $f_{in} = 1.00$  MHz. Display persistence of 1 second is used.


One way to overcome this is to introduce a non-zero static phase error  $\theta_e$  during phase-locked, so that  $\theta_e$  is always larger than the ‘dead-zone’ limit within the frequency range of interest. A simple way to achieve this is to add a shunt resistor across the original series RC network. This is shown in Figure A3. Resistor  $R_B$  acts as a ‘bleeding’ resistor, it will discharge  $C_2$  continuously, so that a constant pulse from the charge-pump is needed to maintain a fixed average dc voltage to the VCO input. Effectively this means a small phase error is required between VCO output and  $V_{in}$  during phase-locked. This resistor value is typically chosen to be  $10R_1$  (4.7 k $\Omega$  in this case). Figure A4 shows the jitter in VCO output disappear after this modification, while Figure A5 compares the VCO and  $V_{in}$  waveforms to show the static phase error that results in the fix voltage pulse of  $V_o$  in Figure 4.

 

**Figure A3** – Introducing the ‘bleeding’ resistor  $R_B$  to eliminate VCO output jitter.

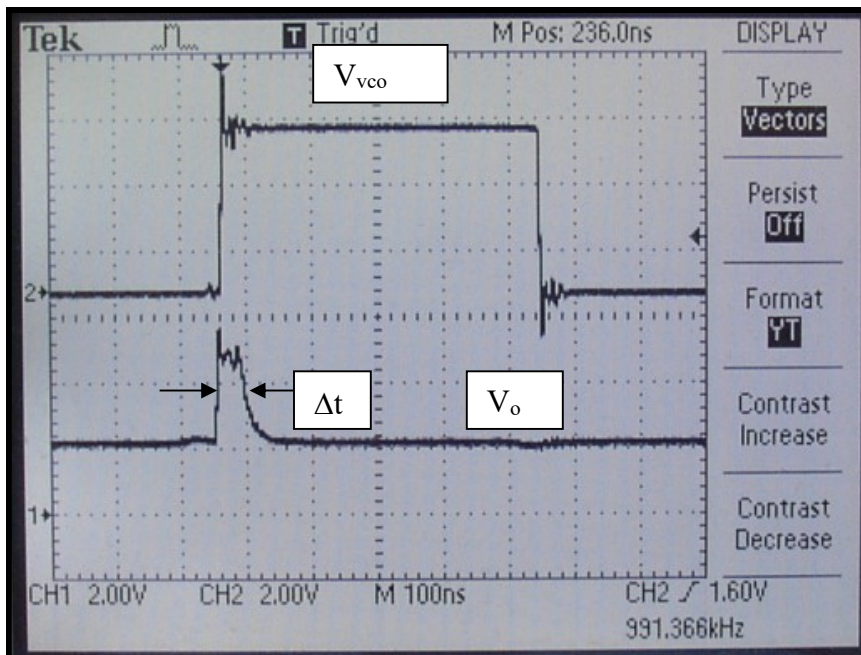


**Figure A4** -  $V_{vco}$  (trigger source) and  $V_o$  waveform, at  $f_{in} = 1.00$  MHz.

 

**Figure A5** -  $V_{vco}$  (trigger source) and  $V_{in}$  waveform, at  $f_{in} = 1.00$  MHz.

Figure A6 shows the comparison of VCO and  $V_{in}$  at  $f_{in} = 1.70$  MHz. Note that the static phase error increases in this case as a broader pulse from the charge-pump is needed to generate a higher dc average voltage from the modified RC network. If the value of  $R_B$  is too large, it is not effective because the required static phase error is still within the 'dead-zone' limit. If  $R_B$  is too small, it will affect the dynamic response of the PLL, moreover this also reduces the lock range (as the maximum frequency trackable by the PLL is limited to  $\theta_e = 180^\circ$ ).

 

**Figure A6** -  $V_{vco}$  (trigger source) and  $V_{in}$  waveform, at  $f_{in} = 1.70$  MHz.